

by compensation


$$V_o(s) = \frac{V_i(s) [R_2 + 1/sC]}{R_1 + R_2 + 1/sC}$$

$$T(s) = \frac{V_o(s)}{V_i(s)}$$


$$T(s) = \frac{R_2 + 1/sC}{R_1 + R_2 + 1/sC} = \frac{1 + R_2 sC}{C(R_1 + R_2)s + 1}$$

Pole $s = -\frac{1}{C(R_1 + R_2)}$

Zero $s = -\frac{1}{R_2 C}$

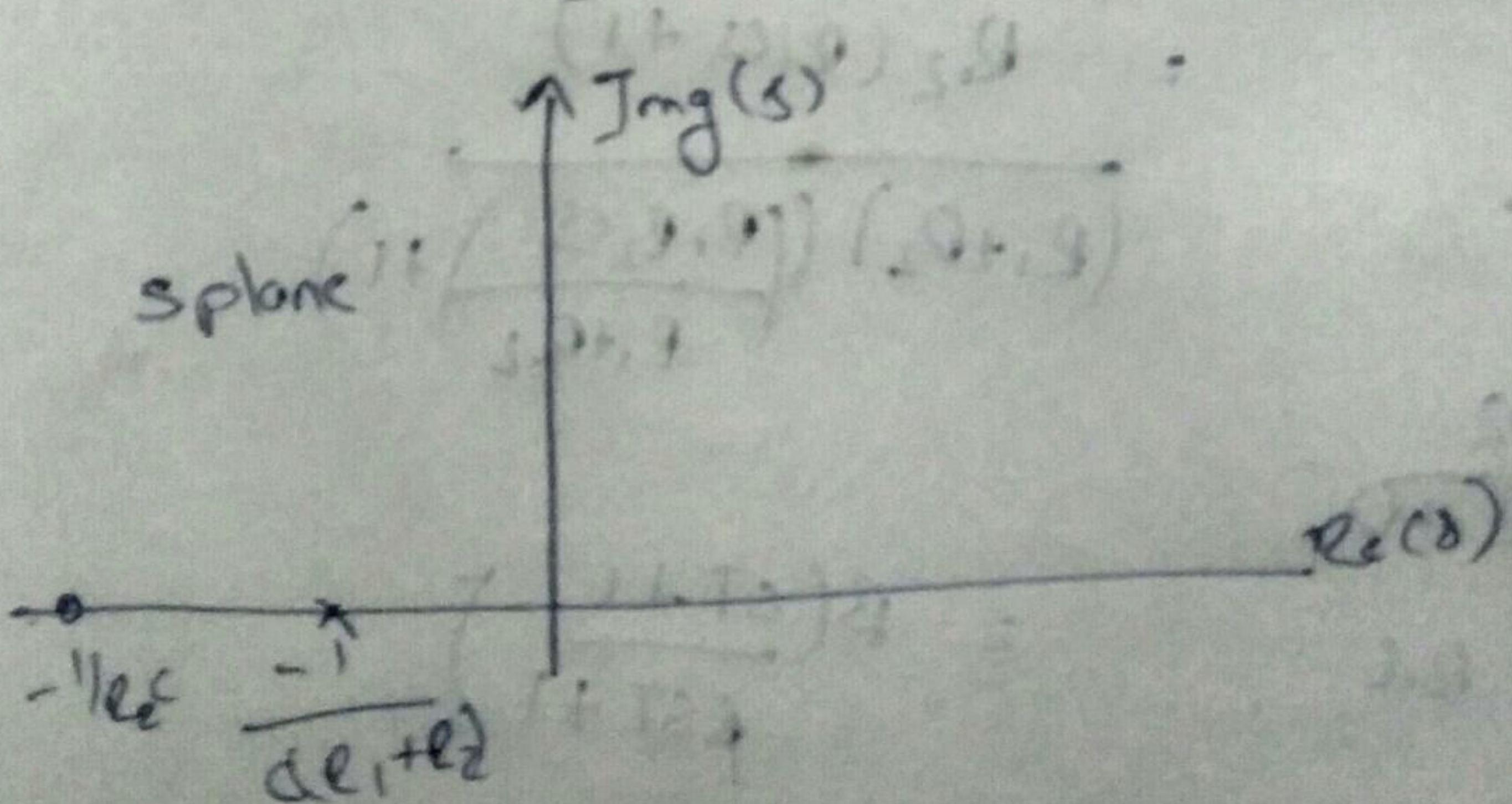

Lead compensator

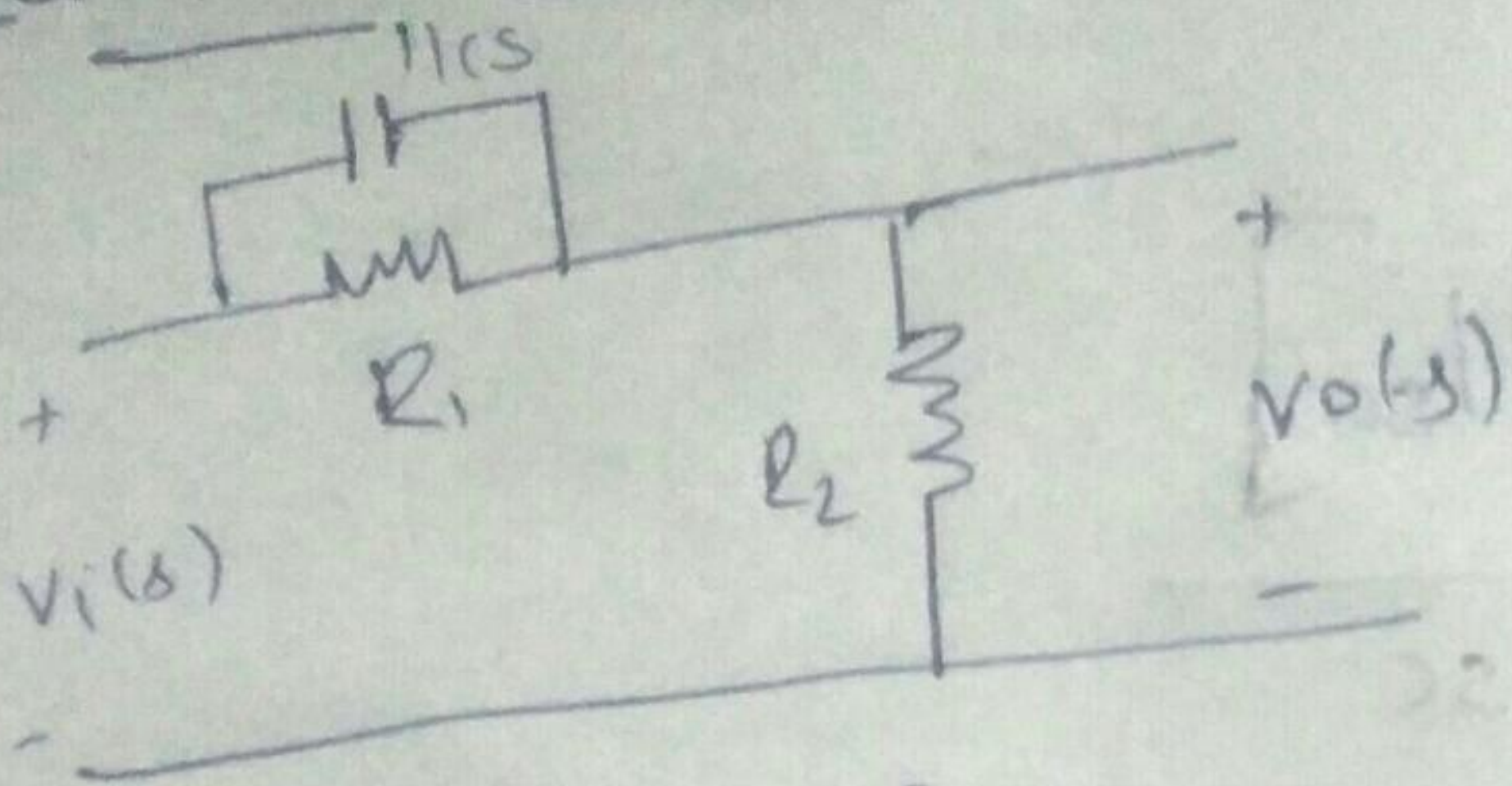

$$\frac{V_o(s)}{V_i(s)} = \frac{R_2}{R_2 + (1/s) \parallel R_1}$$

$$= \frac{R_2}{R_2 + \frac{R_1 \cdot 1/s}{R_1 + 1/s}}$$

$$= \frac{R_2(R_1 s + 1)}{R_2(R_1 s + 1) + R_1}$$


$$= \frac{R_2(R_1 s + 1)}{(R_1 + R_2) \left(\frac{R_1 R_2 s}{R_1 + R_2} + 1 \right)}$$

$$\beta = \frac{R_2}{R_1 + R_2}$$

$$T = R_1 C$$

$$= \beta \left(\frac{sT + 1}{sT + 1} \right)$$

P-controller

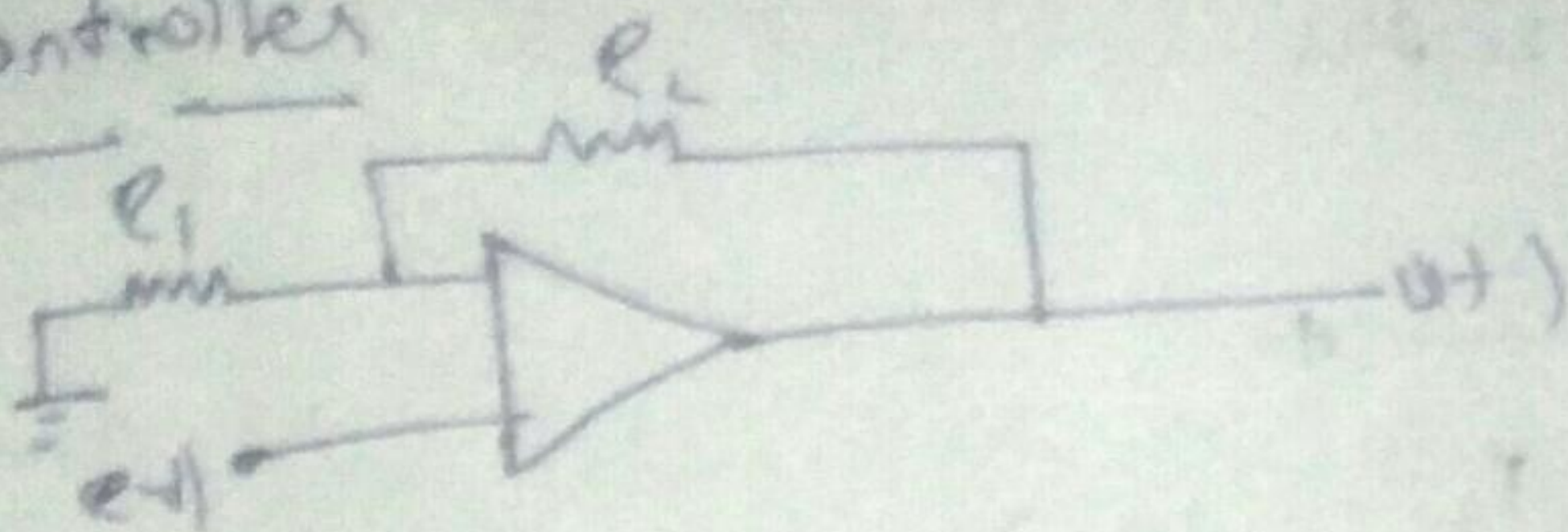


By voltage division rule

$$u(s) = \frac{R_2}{R_1 + R_2} e(s)$$

$$U(s) = \frac{R_1 + R_2}{R_1} E(s)$$

$$\boxed{\frac{U(s)}{E(s)} = \frac{R_1 + R_2}{R_1}}$$

lag lead compensator

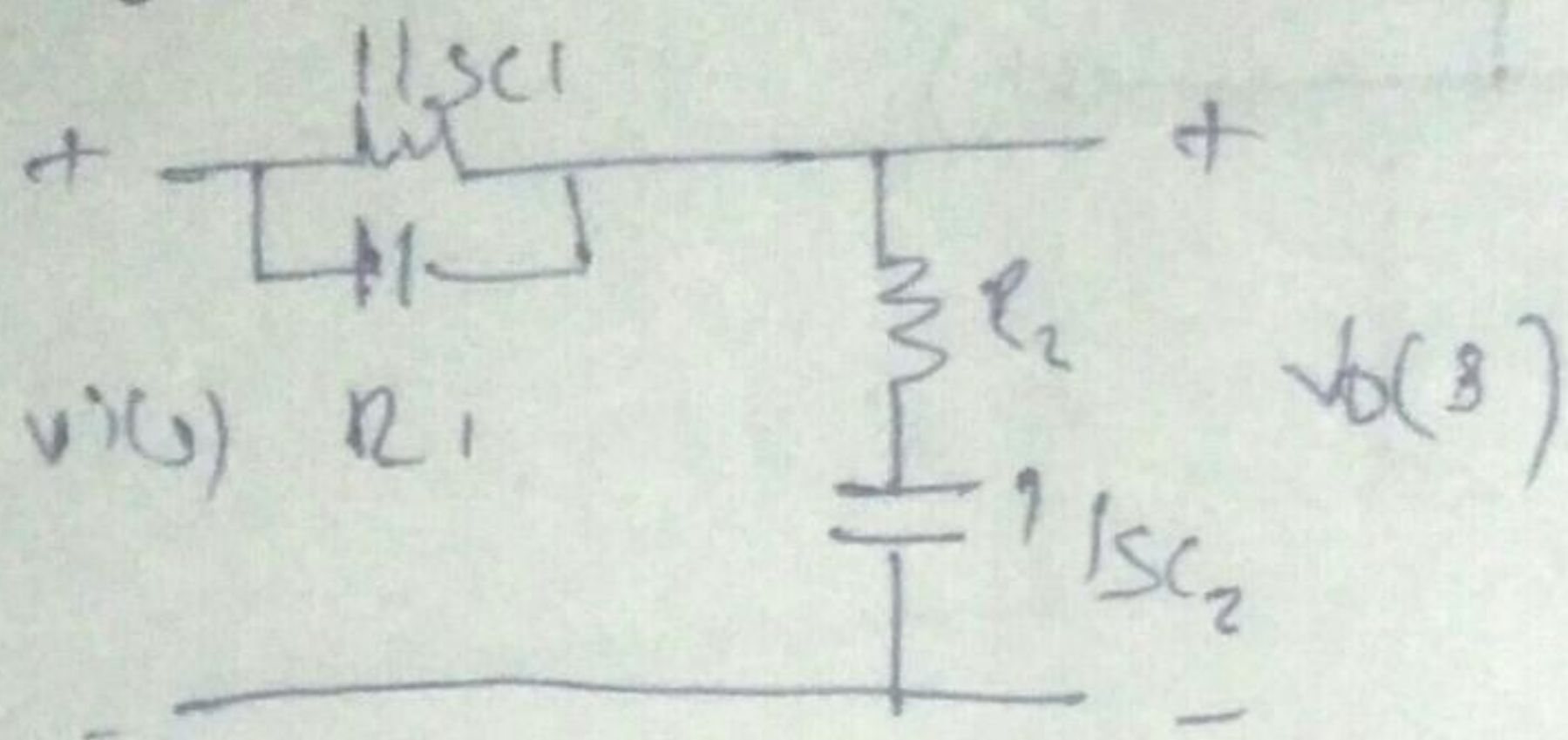

$$V_i(s) = \left(\frac{R_1}{R_1 s C_1 + 1} + \frac{R_2 s C_2 + 1}{s C_2} \right) I(s)$$

$$V_o(s) = \frac{R_2 s C_2 + 1}{s C_2} I(s)$$

$$T F = \frac{V_o(s)}{V_i(s)} = \frac{R_2 s C_2 + 1}{R_2 s C_2 + (R_1 s C_1 + 1)(R_2 s C_2 + 1)}$$


$$T F \text{ lag-lead} = \frac{(R_1 C_1 s + 1)(R_2 C_2 s + 1)}{R_1 R_2 C_1 C_2 s^2 + (R_1 C_1 + R_2 C_2 + R_1 C_2) s + 1}$$

$$\alpha T_1 = R_1 C_1$$


$$R_2 C_2 = \beta T_2 \quad ; \quad R_1 R_2 C_1 C_2 = \alpha \beta T_1 T_2$$

$$T_1 T_2 = R_1 R_2 C_1 C_2$$
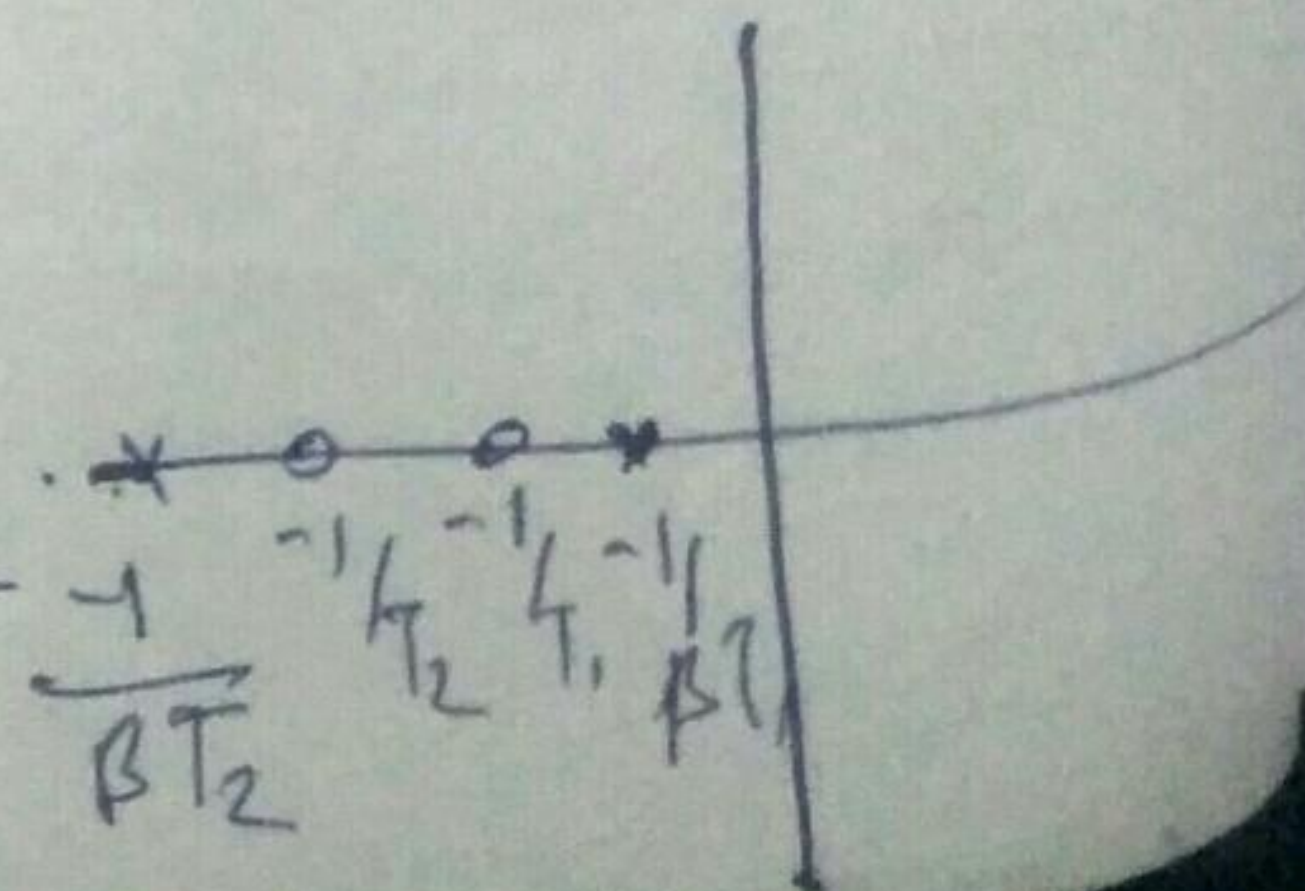
$$T F = \frac{(1 + \alpha T_1 s)(1 + \beta T_2 s)}{(1 + T_1 s)(1 + T_2 s)}$$



PI controller

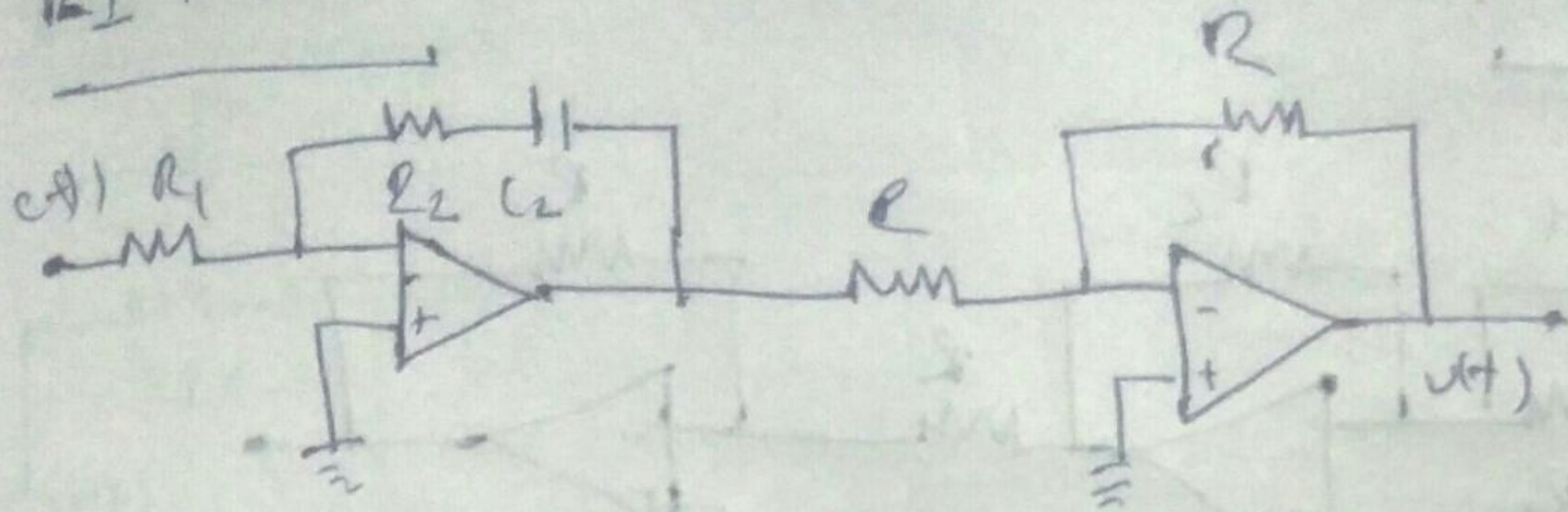

$$u(t) \propto [e(t) + \int e(t) dt] \therefore u(t) = k_p e(t) + \frac{k_p}{T_i} \int e(t) dt$$

where k_p = Proportional gain

T_i = Integral time

$$\frac{U(s)}{E(s)} = k_p \left[1 + \frac{1}{T_i s} \right]$$

$$U(s) = k_p E(s) + \frac{k_p}{T_i} \frac{E(s)}{s}$$

In above example


$$-u(t) = \frac{-e(t)}{R_2} R_2 - \frac{1}{C_2} \int \frac{e(t)}{R_1} dt$$

$$\frac{U(s)}{E(s)} = \frac{R_2}{R_1} \left[1 + \frac{1}{R_2 C_2 s} \right]$$

$$\therefore k_p = \frac{R_2}{R_1}$$

$$T_i = R_2 C_2$$

PD Controller

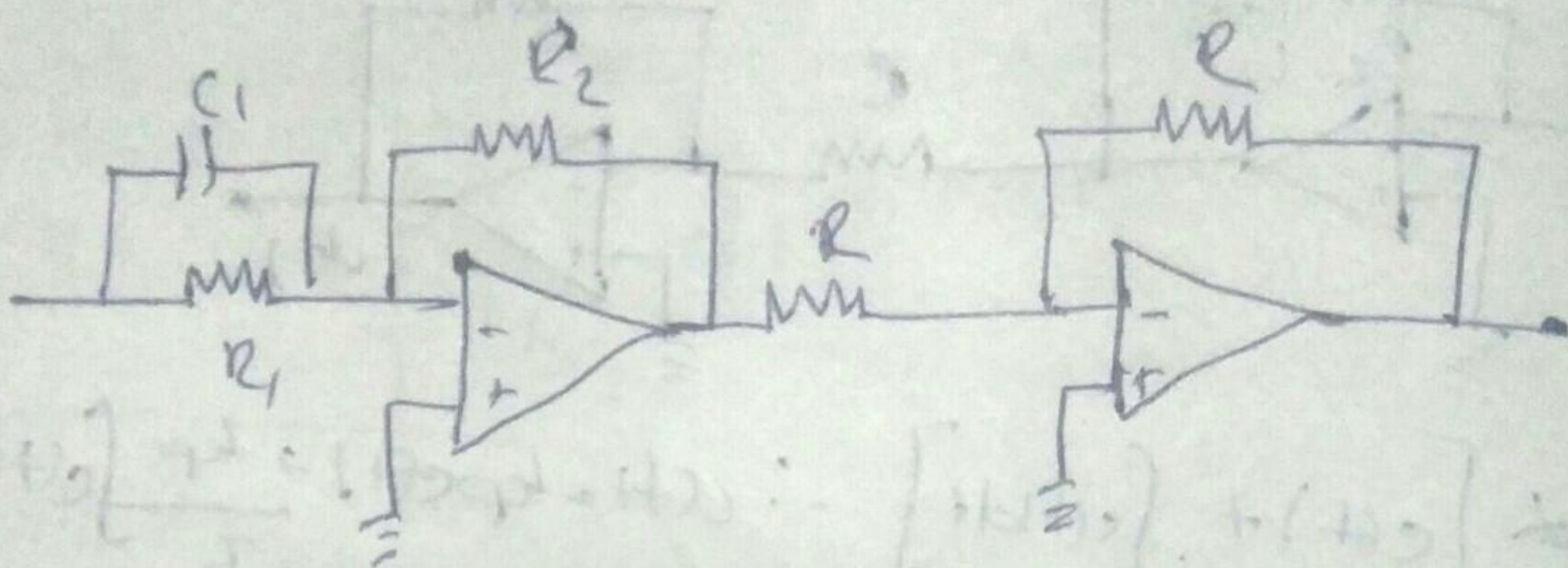

$$U(t) = K_p E(t) + K_p T_d \frac{d}{dt} E(t)$$

$$U(t) = K_p E(t) + K_p T_d \frac{d}{dt} E(t)$$

$$U(s) = K_p E(s) + K_p T_d s E(s)$$

$$\boxed{TF = K_p (1 + T_d s)}$$

Above example


$$-U(t) = \frac{R_2}{R_1} E(t) + R_2 C_1 \frac{d}{dt} E(t)$$

$$U(t) = \frac{R_2}{R_1} E(t) + R_2 C_1 \frac{d}{dt} E(t)$$

$$\frac{U(s)}{E(s)} = \frac{R_2}{R_1} (1 + R_1 C_1 s)$$

$$K_p = \frac{R_2}{R_1} \quad T_d = R_1 C_1$$

PID controller

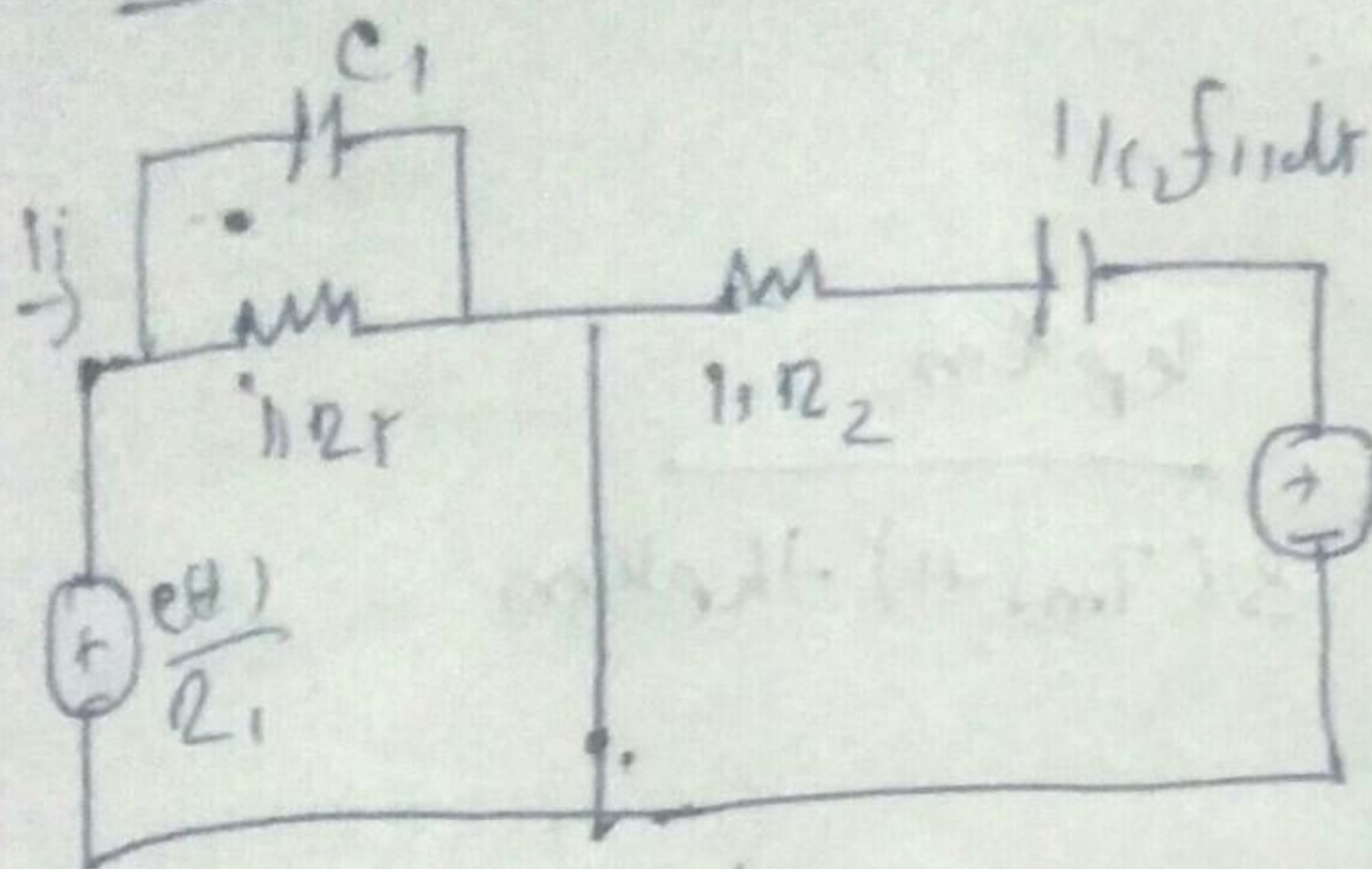

amplifier

$$i_1 = \frac{e(t)}{R_1} + C_1 \frac{d e(t)}{dt}$$

$$I_1(s) = \frac{1}{R_1} E(s) + (s C_1 E(s))$$

$$I_1(s) = \left(\frac{1}{R_1} + C_1 s \right) E(s)$$

$$I_1(s) \left(R_2 + \frac{1}{C_2 s} \right) = -U_1(s)$$

$$-\left[\frac{R_2}{R_1} + \frac{C_1}{C_2} + \frac{1}{R_1 C_2 s} + R_2 C_1 s \right] E(s) = U(s)$$

$$\frac{U(s)}{E(s)} = \frac{R_2}{R_1} \left[\frac{R_2 C_2 + R_1 C_1 + \frac{1}{R_2 C_2 s} + R_1 C_1 s}{R_2 C_2} \right]$$

$$T_1 = R_2 C_2$$

$$K_p = \frac{R_2}{R_1}$$

$$T_d = R_1 C_1$$

$$\frac{R_1 C_1 + R_2 C_2}{R_2 C_2} = 1$$

Servo motor

$$\frac{Q(s)}{Q(s)} = \frac{k_p k_m}{s(T_m s + 1)} \cdot \frac{1}{1 + \frac{k_p k_m}{s(T_m s + 1)}}$$

$$\frac{k_p k_m}{s(T_m s + 1) + k_p k_m}$$

$$1 + G(s)H(s) = 0$$

$$T_m s^2 + s + k_p k_m = 0$$

$$s_{1,2} = \frac{-1 \pm \sqrt{1 - 4 T_m k_p k_m}}{2 T_m}$$

poles of the Transfer function depend on the values of $k_p k_m$ //

$$\left[2.0 \pm \frac{1}{2.0} + \frac{1.0 \pm 1.0}{2.0} \right] = \frac{1.0}{1.0}$$

h) Time domain specifications

$$c/s eqn = s^2 + \frac{s}{T_m} + \frac{k_p k_m}{T_m}$$

$$\omega_n = \sqrt{\frac{k_p k_m}{T_m}}$$

$$2\zeta\omega_n = \frac{1}{T_m}$$

$$\zeta = \frac{1}{2T_m} \sqrt{\frac{T_m}{k_p k_m}}$$

$$\zeta = \frac{1}{2\sqrt{T_m k_p k_m}}$$

$$tr = \frac{\pi - \theta}{\omega_d}$$

$$\omega_d = \omega_n \sqrt{1 - \zeta^2}$$

$$= \frac{\sqrt{4T_m k_p k_m - 1}}{2T_m}$$

$$2T_m$$

$$tr = \frac{2T_m \left[\pi - \frac{\pi}{180} \cos^{-1} \zeta \right]}{\sqrt{4T_m k_p k_m - 1}}$$

$$\sqrt{4T_m k_p k_m - 1}$$

$$t_p = \frac{2\pi T_m}{\sqrt{4T_m k_p k_m - 1}}$$

$$\sqrt{4T_m k_p k_m - 1}$$

$$M_0 = e^{-\frac{\pi \epsilon_1}{\sqrt{1-\epsilon_1^2}}}$$

$$= e^{-\frac{\pi \cdot \frac{1}{2} \sqrt{7} \text{ km km}^{-1}}{\sqrt{1 - \frac{1}{4 \cdot 7 \text{ km km}^{-1}}}}}$$

$$M_0 = e^{-\frac{\pi}{\sqrt{4 \text{ km km}^{-1}}}}$$

Settling Time:

$$2\% \text{ EB det} = \frac{4}{\epsilon_1 \omega_n} = 4 \left(\frac{1}{\frac{1}{2} \text{ km}^{-1}} \right) = 8 \text{ km}$$

$$5\% \text{ EB det} = \frac{3}{\epsilon_1 \omega_n} = \frac{3}{\frac{1}{2} \text{ km}^{-1}} = 6 \text{ km}$$

Difference between First order and Second order Systems

1st order

- In the system in which as input changes, output also changes but not immediately as called first order system.
- The system takes some delay but without oscillations. [does not exhibit ripples]

2nd order

- 1 & 2 independent energy storage element.
- may or ~~not~~ may not exhibit oscillatory

behaviour

- Natural frequency and damping ratio play an important role.