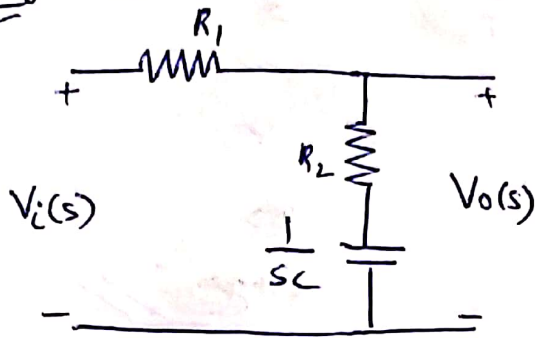


Q1] a) Log Compensator




$$\frac{V_o(s)}{V_i(s)} = \frac{R_2 + \frac{1}{Cs}}{R_1 + R_2 + \frac{1}{Cs}} = \frac{1 + R_2Cs}{(R_1 + R_2)Cs + 1}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{R_2 \left(s + \frac{1}{R_2C} \right)}{(R_1 + R_2) \left[s + \frac{1}{(R_1 + R_2)C} \right]} = \frac{s + \frac{1}{R_2C}}{\alpha \left(s + \frac{1}{(R_1 + R_2)C} \right)}$$

$$\alpha = \frac{R_1 + R_2}{R_2} > 1 \text{ for log compensator}$$
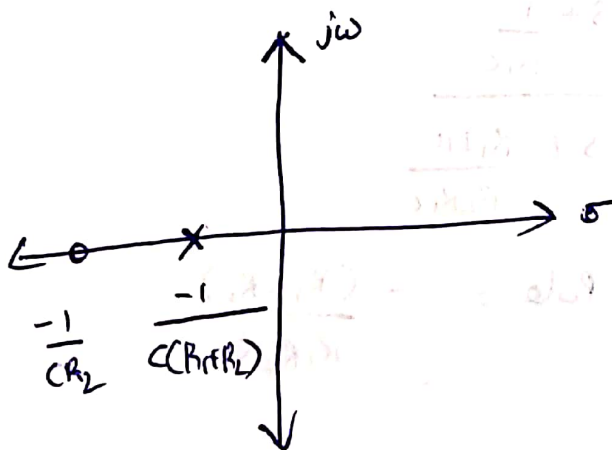
$$\text{Zero} = -\frac{1}{R_2C} \quad \text{Pole} = -\frac{1}{(R_1 + R_2)C}$$



$$\tau = R_2C$$



$$\alpha\tau = (R_1 + R_2)C$$

$$\frac{1}{\alpha\tau} = \frac{1}{(R_1 + R_2)C}$$

$$\because \alpha > 1 \Rightarrow \frac{1}{\alpha\tau} < \frac{1}{\tau}$$

The pole $-\frac{1}{\alpha\tau}$ is nearer to origin $\leftarrow \Rightarrow -\frac{1}{\alpha\tau} > -\frac{1}{\tau}$

(b) Lead compensator

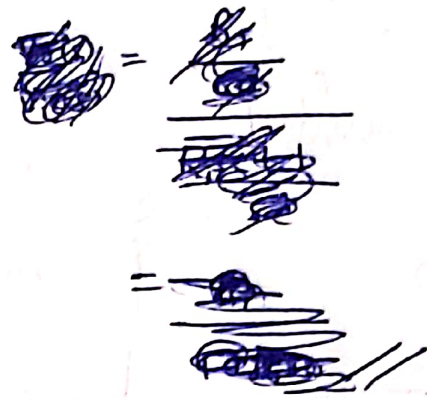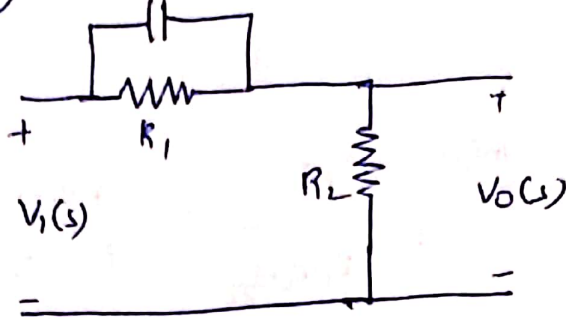

$$\frac{V_o(s)}{V_i(s)} = \frac{R_2}{R_2 + \frac{R_1}{1 + R_1 s C}} = \frac{R_2 (1 + R_1 s C)}{R_1 + R_2 + s R_1 R_2 C}$$


$$TF = \frac{R_2 + R_1 R_2 s C}{R_1 + R_2 + s R_1 R_2 C}$$

$$= \frac{R_2 R_1 C \left(s + \frac{1}{R_1 C} \right)}{R_1 R_2 C \left(s + \frac{R_1 + R_2}{R_1 R_2 C} \right)}$$

$$= \frac{s + \frac{1}{R_1 C}}{s + \frac{R_1 + R_2}{R_1 R_2 C}}$$


$$\text{Zero} = -\frac{1}{R_1 C}$$
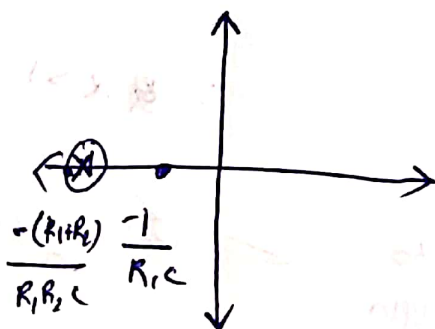
$$\text{Pole} = -\frac{(R_1 + R_2)}{R_1 R_2 C}$$



Here the pole is far away from the origin
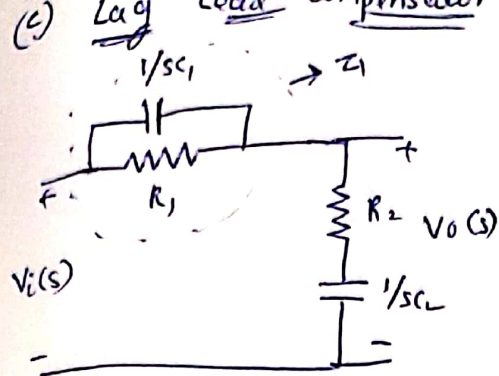
$$\therefore \frac{(R_1 + R_2)}{R_1 R_2 C} \gg \frac{1}{R_1 C}$$



$$Z_1 = \frac{R_1 \left(\frac{1}{sC_1} \right)}{R_1 + \frac{1}{sC_1}} = \frac{R_1}{1 + sR_1C_1}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{R_2 + \frac{1}{sC_2}}{R_2 + \frac{1}{sC_2} + \frac{R_1}{1 + sR_1C_1}}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{\left(\frac{1 + sR_2C_2}{sC_2} \right)}{\left[\frac{R_1sC_2 + R_2(sC_2)(1 + sR_1C_1) + 1 + sR_1C_1}{(sC_2)(1 + sR_1C_1)} \right]}$$

$$TF = \frac{(1 + sR_1C_1)(1 + sR_2C_2)}{s^2R_1R_2C_1C_2 + s(R_1C_1 + R_1C_2 + R_2C_2) + 1}$$

$$= \frac{1 + s^2R_1R_2C_1C_2 + sR_2C_2 + sR_1C_1}{s^2R_1R_2C_1C_2 + s(R_1C_1 + R_1C_2 + R_2C_2) + 1}$$

Zeros:-

$$s^2(R_1R_2C_1C_2) + s(R_2C_2 + R_1C_1) + 1 = 0$$

$$s = \frac{- (R_1R_2C_1C_2) \pm \sqrt{(R_1C_1 + R_2C_2)^2 - 4R_1R_2C_1C_2}}{2R_1R_2C_1C_2}$$

Poles:-

$$s^2R_1R_2C_1C_2 + s(R_1C_1 + R_1C_2 + R_2C_2) + 1 = 0$$

$$s = \frac{- (R_1C_1 + R_1C_2 + R_2C_2) \pm \sqrt{(R_1C_1 + R_1C_2 + R_2C_2)^2 - 4R_1R_2C_1C_2}}{2R_1R_2C_1C_2}$$

$$TF = \frac{(R_1C_1s + 1)(R_2C_2s + 1)}{R_1R_2C_1C_2s^2 + (R_1C_1 + R_1C_2 + R_2C_2)s + 1}$$


$$= \frac{\left(s + \frac{1}{R_1C_1}\right)\left(s + \frac{1}{R_2C_2}\right)}{s^2 + s\left(\frac{1}{R_1C_1} + \frac{1}{R_2C_2} + \frac{1}{R_2C_1}\right) + \frac{1}{R_1R_2C_1C_2}}$$

$$\text{Let } \alpha T_1 = R_1 C_1$$


$$\beta T_2 = R_2 C_2$$

$$\Rightarrow R_1 R_2 C_1 C_2 = T_1 T_2 \times \alpha \beta$$
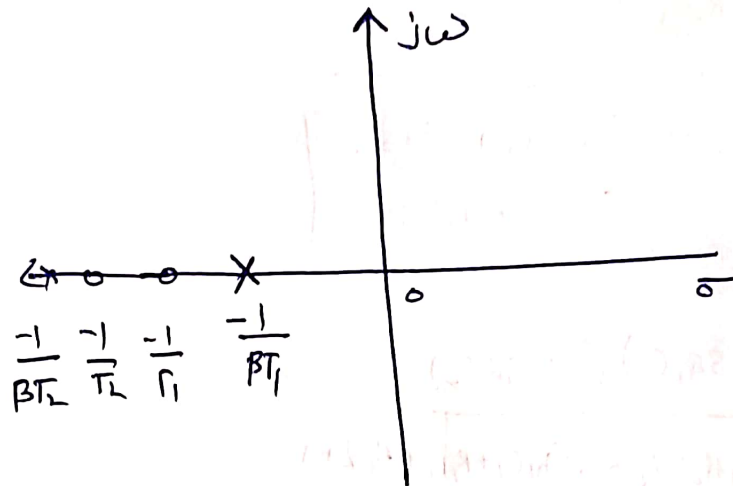
$$\Rightarrow TF = \frac{(1 + \alpha T_1 s)(1 + \beta T_2 s)}{(1 + T_1 s)(1 + T_2 s)}$$



(d) P-Controller

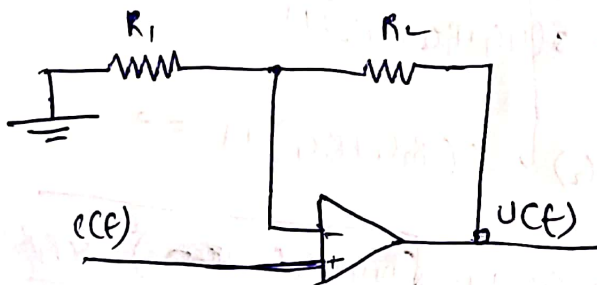

The voltage in inverting terminal is same as the one in non-inverting due to virtual short.

$$\frac{e(t) - 0}{R_1} + \frac{u(t) - u(t)}{R_2} = 0$$

$$e(t) \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{u(t)}{R_2}$$

$$e(t) = u(t) \times \frac{R_2}{R_1 + R_2}$$

By using Laplace Transform


$$C(s) = \frac{(R_1 + R_2)}{R_1} U(s)$$

$$\frac{U(s)}{C(s)} = \frac{R_1}{R_1 + R_2}$$

The TF is constant in P-controller.

~~P-controller~~

(e) PI Controller

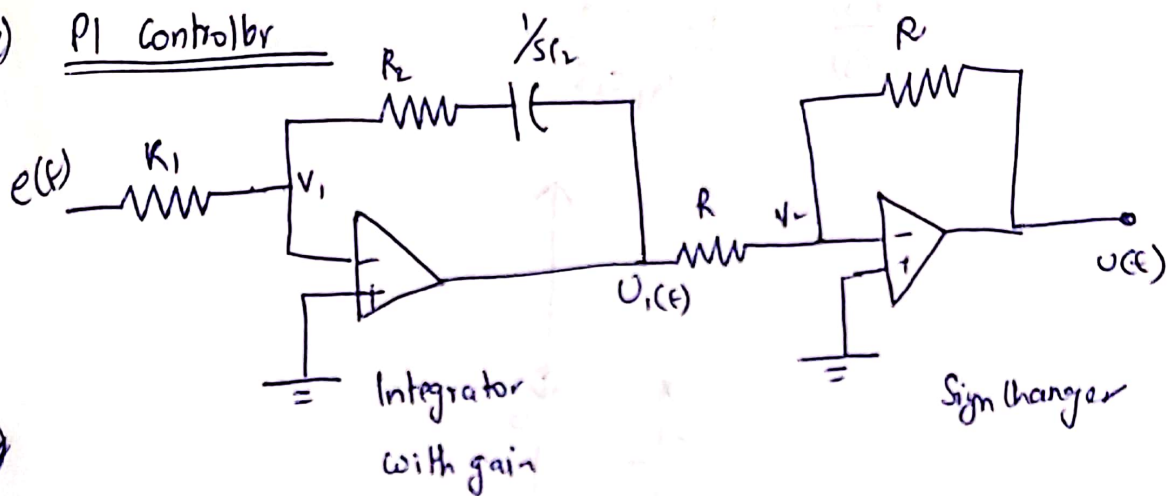

Due virtual short $V_1 = V_2 = 0$

At V_1 using nodal

$$\frac{V_1 - U_1(s)}{R_2 + \frac{1}{sC_2}} + \frac{V_1 - E(s)}{R_1} = 0$$

$$-\frac{E(s)}{R_1} - \frac{U_1(s)}{R_2 + \frac{1}{sC_2}} = 0 \quad [V_1 = 0]$$

$$\frac{E(s)}{R_1} = -\frac{U_1(s)}{R_2 + \frac{1}{sC_2}} \Rightarrow \frac{U_1(s)}{E(s)} = \frac{-(R_2 + \frac{1}{sC_2})}{R_1}$$

- ①


$$\frac{V_2 - U_1(s)}{R} + \frac{V_2 - U(s)}{R} = 0$$

$$U_1(s) = -U(s) \quad \text{--- (2)}$$


Subbing (1) in (2)

$$\Rightarrow \boxed{\frac{U(s)}{E(s)} = \frac{R_2}{R_1} + \frac{1}{R_1 C_2 s}}$$
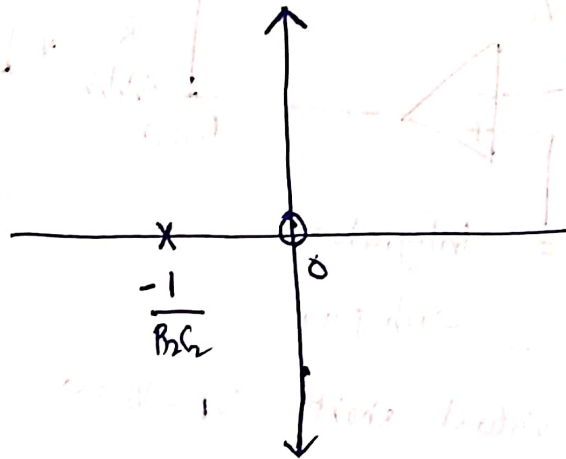
$$\frac{U(s)}{E(s)} = \frac{R_2 C_2 s + 1}{R_1 C_2 s}$$



(f) PD Controller

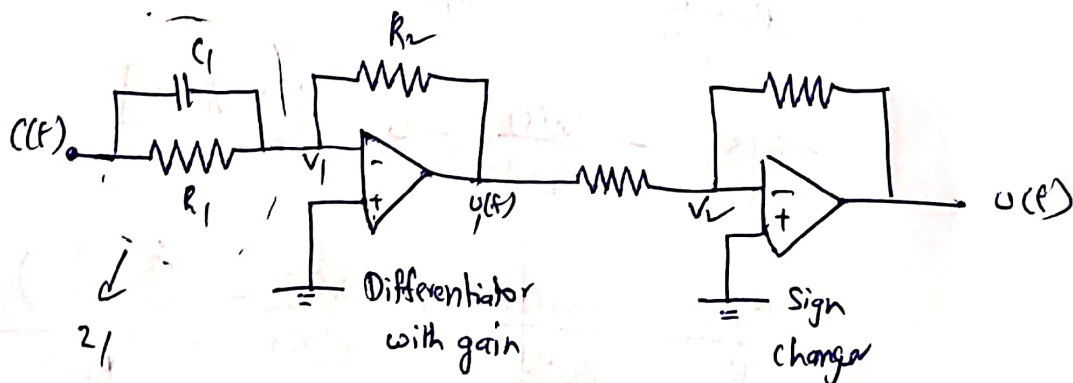

$$z_1 = \frac{k_1 \left(\frac{1}{C_1 s} \right)}{R_1 + \frac{1}{C_1 s}} = \frac{k_1}{R_1 C_1 s + 1}$$

$V_1 = V_2 = 0$ Due to virtual short

$$\frac{0 - E(s)}{\frac{R_1}{R_1 C_1 s + 1}} + \frac{0 - U_1(s)}{R} = 0$$

$$\frac{-R(R_1 C_1 s + 1) E(s)}{R_1} = U_1(s) \quad \text{--- (1)}$$

$$\frac{0 - U_1(s)}{R} + \frac{0 - U(s)}{R} = 0$$


$$\boxed{U_1(s) = U(s)} \quad \text{--- (2)}$$

Subbing (1) in (2)


$$+\left(\frac{R_2}{R_1}\right)(R_1 C_1 s + 1) E(s) = U(s)$$

$$\frac{U(s)}{E(s)} = \frac{R_2}{R_1} (R_1 C_1 s + 1)$$
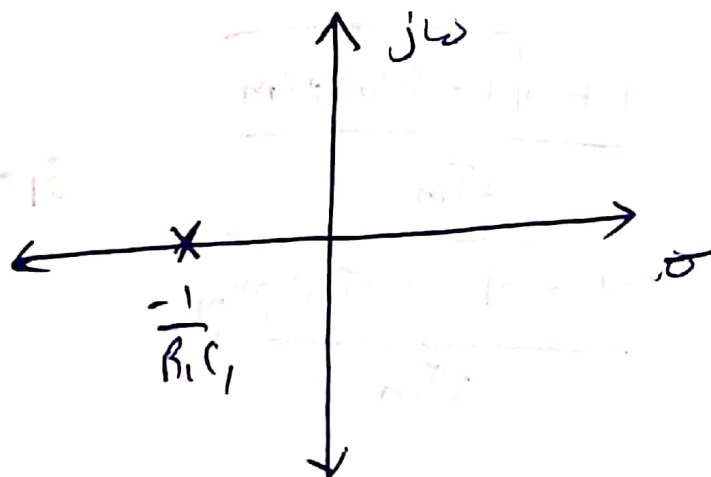
$$\frac{U(s)}{E(s)} = R_2 C_1 \left(s + \frac{1}{R_1 C_1} \right)$$



(g) Servo Motor

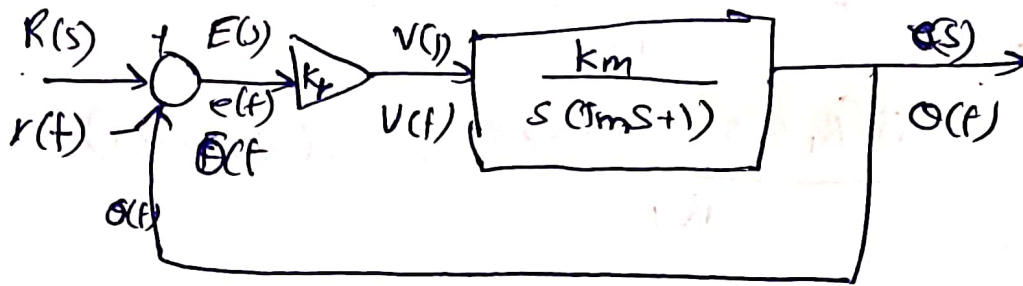

$$\frac{R(s)}{\Theta(s)} = \frac{\frac{K_p K_m}{s(T_m s + 1)}}{1 + \frac{K_p K_m}{s(T_m s + 1)}} = \frac{K_p K_m}{s(T_m s + 1) + K_p K_m}$$

Characteristic eqn: ~~$s(T_m s + 1) + K_p K_m = 0$~~

$$1 + G(s)H(s) = 0$$

$$T_m s^2 + s + K_p K_m = 0$$

$$s = \frac{-1 \pm \sqrt{1 - 4T_m K_p K_m}}{2T_m}$$

$$s_1 = \frac{-1 + \sqrt{1 - 4T_m K_p K_m}}{2T_m}$$

$$s_2 = \frac{-1 - \sqrt{1 - 4T_m K_p K_m}}{2T_m}$$

$$s_1 > s_2$$

n/w

(H) Time domain ~~spec~~ specification

$$TP = \frac{K_p \cdot K_m}{s^2 T_m + s + K_p K_m} = \frac{K_p K_m / T_m}{s^2 + \frac{1}{T_m} s + \frac{K_p K_m}{T_m}} = \frac{\omega_n^2}{s^2 + 2\zeta \omega_n s + \omega_n^2}$$

$$\omega_n^2 = \frac{K_p K_m}{T_m}$$

$$2\zeta \omega_n = \frac{1}{T_m}$$

$$\zeta = \frac{1}{2\sqrt{T_m K_p K_m}}$$

$$t_r = \frac{\pi - \tan^{-1} \left(\frac{\sqrt{1-\zeta^2}}{\zeta} \right)}{\omega_n \sqrt{1-\zeta^2}} = \frac{\pi - \tan^{-1} \left[\frac{\sqrt{4K_p K_m T_m - 1}}{2K_p K_m} \right]}{2K_p K_m}$$

$$t_d = \frac{1 + 0.7\zeta}{\omega_n} = \frac{\sqrt{T_m K_p K_m} + 0.55}{K_p K_m}$$

$$t_p = \frac{\pi}{\omega_d} = \frac{\pi}{\omega_n \sqrt{1-\zeta^2}} = \frac{\pi}{2K_p K_m}$$

Peak overshoot $M_p = e^{-\frac{\zeta \pi}{\sqrt{1-\zeta^2}}}$

$$= e^{-\frac{\pi}{\sqrt{4K_p K_m T_m - 1}}}$$

$$t_s = \frac{4}{\zeta \omega_n} = \frac{4}{\frac{1}{2T_m}} = 8T_m \quad (2\% \text{ error})$$

for 5% error

$$t_s = \frac{3}{\zeta \omega_n} = 6T_m$$

Q2] \rightarrow In first order system, there is only one independent energy storage element present, whereas in second order there are two

\rightarrow The response of first order doesn't exhibit ripples irrespective of the pole position.

\rightarrow Second order system may (or) may not exhibit oscillatory behaviour.